

Contents

1	Introduction	1
2	Low-power EDA Technologies	3
	<i>E. Macii and R. Zafalon</i>	
2.1	Introduction and Background	4
2.2	Low-Power Design Flow	6
2.3	Low-Power Design Technologies	7
2.3.1	Dynamic Power Control	8
2.3.2	Leakage Power Control	29
2.4	Conclusions	40
2.5	Bibliography	40
3	Extensible and Configurable Processors for SoC Design	45
	<i>Jari Nurmi, Steve Leibson, Fabio Campi, and Christian Panis</i>	
3.1	Introduction	46
3.2	Accelerating Single-Processor Cores – a Co-Processor Approach	47
3.2.1	COFFEE RISC Core	47
3.2.2	Reconfigurable Algorithm Accelerator	49
3.2.3	Mapping Algorithms on RAA	52
3.3	Scalable Instruction-Word VLIW DSP Architecture	55
3.3.1	xDSPcore	58
3.3.2	DSPxPlore	59
3.3.3	Summary	66
3.4	Extensible RISC Processor – Xtensa	66
3.4.1	Xtensa Configurable Registers and Register Files	68
3.4.2	The Xtensa Program Counter	68
3.4.3	Memory Address Space	70
3.4.4	Configurable Byte Ordering	70

CONTENTS

3.4.5	Fast Endian Conversion with One Instruction Extension	71
3.4.6	The TIE Language	74
3.4.7	Improving Application Performance using TIE	74
3.4.8	Adding SIMD Instructions using TIE	78
3.4.9	Adding FLIX Instructions using TIE	79
3.5	Run-Time Reconfigurable DSP RISC Processor	80
3.5.1	XiRisc: a VLIW Processor	83
3.5.2	Pipelined Configurable Gate Array (PiCoGA)	85
3.5.3	Software Development Flow	89
3.5.4	Results	92
3.6	Conclusions – The Future of SoC Design	94
3.7	Bibliography	96
4	UWB radio in Distributed Wireless Networks	99
	<i>M.-G. Di Benedetto, G. Giancola, and D. Domenicali</i>	
4.1	Introduction	99
4.2	The UWB Radio Signal and spectral characteristics	101
4.3	Power issues and current standardization trends	104
4.4	Multi User Interference in Impulse Radio UWB Networks	107
4.5	Ranging and Positioning in UWB Networks	111
4.6	Medium Access Control for UWB networks	114
4.7	Location-Aware Routing in UWB networks	116
4.8	Introducing cognitive principles in UWB networks	118
4.9	Bibliography	128
5	Advances on Analog Filters for Telecommunications	131
	<i>A. Baschirotto, S. D’Amico, and M. De Matteis</i>	
5.1	Introduction	132
5.2	Receiver Architectures for Silicon Implementation	133
5.3	The base-band channel selection filter	135
5.4	Active RC filters: the Rauch cell case	136
5.4.1	A Rauch cell design example	137
5.5	The Active- G_m -RC Low-Pass Cell	139
5.5.1	A design example: a fourth-order reconfigurable UMTS/WLAN filter	141
5.5.2	Automatic design toolbox	148
5.6	A source-follower-based continuous-time filter	152
5.6.1	A design example: a fourth-order filter for WLAN	153
5.7	The G_m - G_m -C Filter	158

5.7.1	A design example: a baseband filter for a UWB node	160
5.8	Comparison between the different filter techniques	162
5.9	Conclusions	162
5.10	Bibliography	164
6	Time-Continuous Delta-Sigma A/D Converters	169
	<i>A. Buhmann, M. Keller, M. Ortmanns, F. Gerfers, and Y. Manoli</i>	
6.1	Introduction	170
6.2	Basics	171
6.2.1	Sampling and Quantization	171
6.2.2	Nyquist Rate, Oversampling and Noise-Shaping Converters	172
6.2.3	Performance Increase in $\Sigma\Delta$ Modulators	173
6.2.4	Stability Constraints and Scaling	174
6.2.5	CT Loop-Filter Synthesis	175
6.3	Architectures and Implicit Anti-Aliasing Feature	177
6.3.1	Single-Stage Architectures	177
6.3.2	Multi-Stage/Cascaded Architectures	182
6.4	Non-Idealities and Correction Techniques	187
6.4.1	Different Error Locations or Input Referred Non- Idealities	187
6.4.2	Errors of the Feedback DAC	188
6.4.3	Errors of the Filters	192
6.4.4	Errors of the Internal Quantizer	196
6.5	Recent Implementations of CT $\Sigma\Delta$ Modulators	196
6.5.1	CT Loop-Filter Implementation	196
6.5.2	Single- and Multi-bit Quantizer and Feedback DAC Realization	199
6.5.3	Implementation Example I: A 12-Bit 25kHz 1.5V CT $\Sigma\Delta$ Modulator	201
6.5.4	Implementation Example II: A CT $\Sigma\Delta$ Modulator with SCR-Feedback	203
6.5.5	Implementation Example III: A 70-mW 300-MHz CMOS Continuous-Time $\Sigma\Delta$ ADC With 15-MHz Bandwidth and 11 Bits of Resolution	204
6.5.6	Implementation Example IV: A Cascaded CT $\Sigma\Delta$ Modulator with 67dB Dynamic Range in 10MHz Bandwidth	207
6.6	Conclusion	209
6.7	Bibliography	210

CONTENTS

7	ESD Protection Design in nano CMOS	217
	<i>M.-D. Ker</i>	
7.1	Introduction to Electrostatic Discharge (ESD)	218
7.1.1	ESD Standards and Models	218
7.1.2	ESD Testing	223
7.1.3	ESD Testing for HBM / MM	223
7.2	Design Techniques of ESD Protection Circuit	231
7.2.1	Basic ESD Protection Concept	231
7.2.2	Turn-on Uniformity of ESD Protection Devices	233
7.2.3	ESD Implantation and Silicide Blocking	235
7.2.4	Some ESD Protection Guidelines	237
7.3	Whole-Chip ESD Protection Design	238
7.3.1	Power-Rail ESD Clamp Circuit	241
7.3.2	Location of Power-Rail ESD Clamp Circuit	245
7.3.3	Protection for ICs with Separated Power Lines	247
7.4	ESD Protection for Mixed-Voltage I/O Interface	248
7.4.1	Mixed-Voltage I/O	248
7.4.2	ESD Design Constraints in Mixed-Voltage I/O	251
7.4.3	ESD Protection Design for Mixed-Voltage I/O	255
7.4.4	High-Voltage-Tolerant Power-Rail ESD Clamp Circuit	264
7.5	Summary	268
7.6	Bibliography	270
	List of Figures	281
	List of Tables	291